



Name, Surname :
 Number :
 Course Code : BLM1612
 Course Name : CIRCUIT THEORY
 Exam : ☐ Quiz ☒ Midterm ☐ Final
 Date : 15.12.2016

Please make sure to write your name and student number on each paper that you have used

Question Number	1	2	3	4	5	6	7	8	Total
Mark									

Note: Exam duration is 120 minutes only and max 2 papers can be used.

QUESTIONS

- A stereo system draws 1.8 A at 120 V. The audio output power is 50 W.
 - How much power is lost in the form of heat in the system?
 - What is the efficiency of the system?
- Determine R_1 for the circuit in Fig. 1

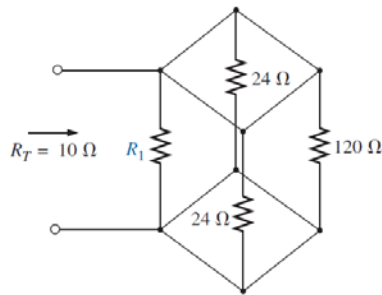


Fig. 1

- The voltage across a 1 F capacitor is shown on the waveform of Fig. 2. Compute and sketch the current for the time interval $0 < t < 12$ s.

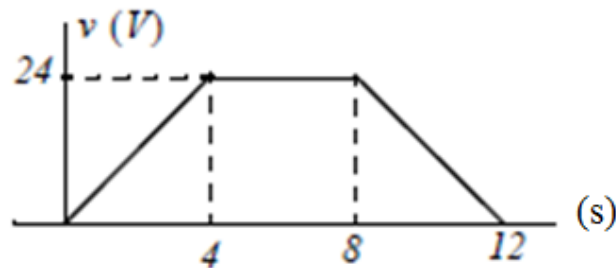


Fig. 2

- Reduce the circuit in Fig. 3 to the fewest number of components.

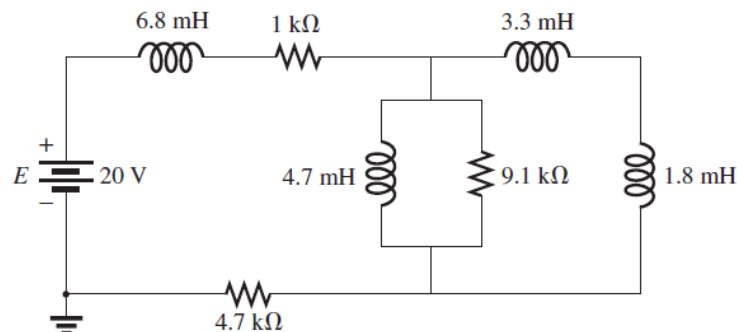


Fig. 3

5. In the circuit of Fig. 4, calculate the phasor voltage V_{OUT2} . ($V_{IN} = -j5 \text{ V}$)

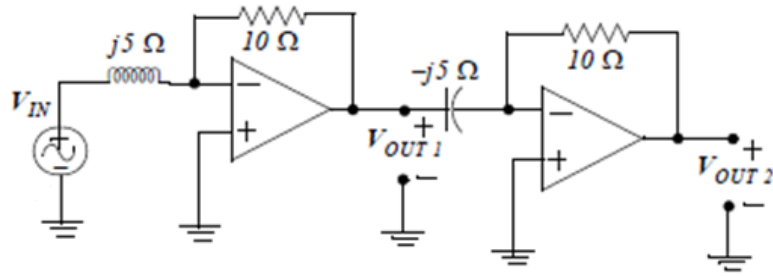


Fig. 4

6. Write loop equations to compute $i_C(t)$ for the circuit of Fig. 5 given that $v_s(t) = 12 \sin(100t - 45^\circ) \text{ V}$.

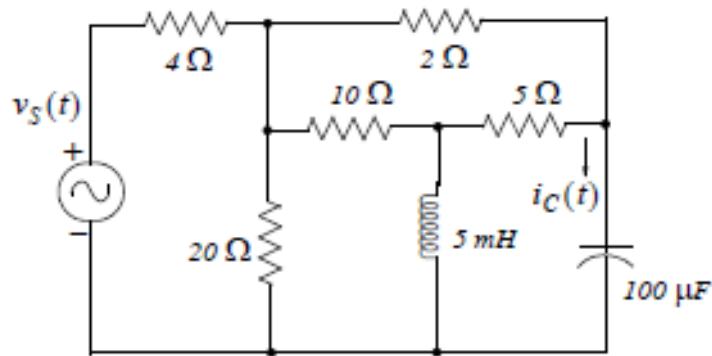


Figure 5

7. The circuit is given in Fig. 6. Find power dissipated in $R_5 = 36 \text{ k}\Omega$ using Thevenin equivalent of the circuit

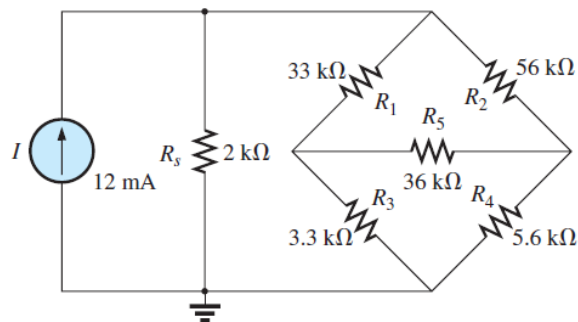


Fig. 6

8. In the circuit of Fig. 7, Switch S_1 has been closed for a long time while Switch S_2 has been open for a long time. Switch S_1 opens and Switch S_2 closes at $t=0$. In how many second after $t=0$ has the

- Voltage $v(t)$ has reached half of its initial value?
- Energy stored in C has reached $\frac{3}{4}$ of its initial value

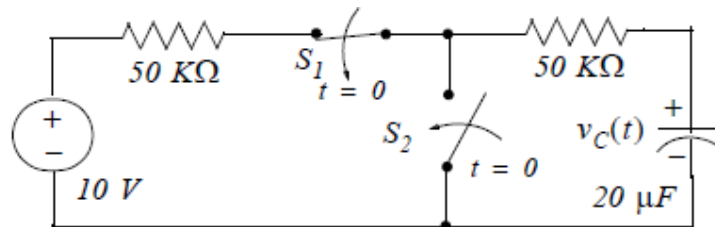


Fig. 7

ANSWERS

①. a) $P_{in} = V \cdot I = 120 \times 1,8 = \underline{216 \text{ W.}}$

$$P_{in} = P_{loss} + P_{out}$$

$$166 = P_{loss} + 50 \Rightarrow P_{loss} = 216 - 50 = 166 \text{ W.}$$

b.) $\eta \% = \frac{P_{out} \times 100}{P_{in}} = \frac{50 \times 100}{216} = 0,2315 \times 100 = \underline{\underline{23,15 \%}}$

② $R_T = R_1 \parallel 24 \parallel 24 \parallel 120$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{24} + \frac{1}{24} + \frac{1}{120}$$

$$\frac{1}{10} = \frac{1}{R_1} + 0,0416 + 0,0416 + 0,00833$$

$$\frac{1}{R_1} = 0,1 - 0,09167 = 0,00833 \text{ S}$$

$$R_1 = 120 \text{ } \Omega$$

③ $i_c = C \cdot \frac{dv_c}{dt} = C \cdot \text{slope}$

for $0 < t < 4 \text{ s.}$

$$\text{slope} = \frac{24 - 0}{4} = 6 \text{ V/s}$$

$$i_c = C \cdot \text{slope} \Big|_0^4 = 1 \times 6 = 6 \text{ A.}$$


for $4 < t < 8 \text{ s}$

$$\text{slope} = 0 \Rightarrow i_c = C \cdot \text{slope} \Big|_4^8 = 1 \times 0 = 0 \text{ V}$$


for $8 < t < 12$

$$\text{slope} = \frac{0 - 24}{12 - 8} = -6 \text{ V/s}$$

$$i_c = C \cdot \text{slope} \Big|_8^{12} = 1 \times (-6) = -6 \text{ V.}$$

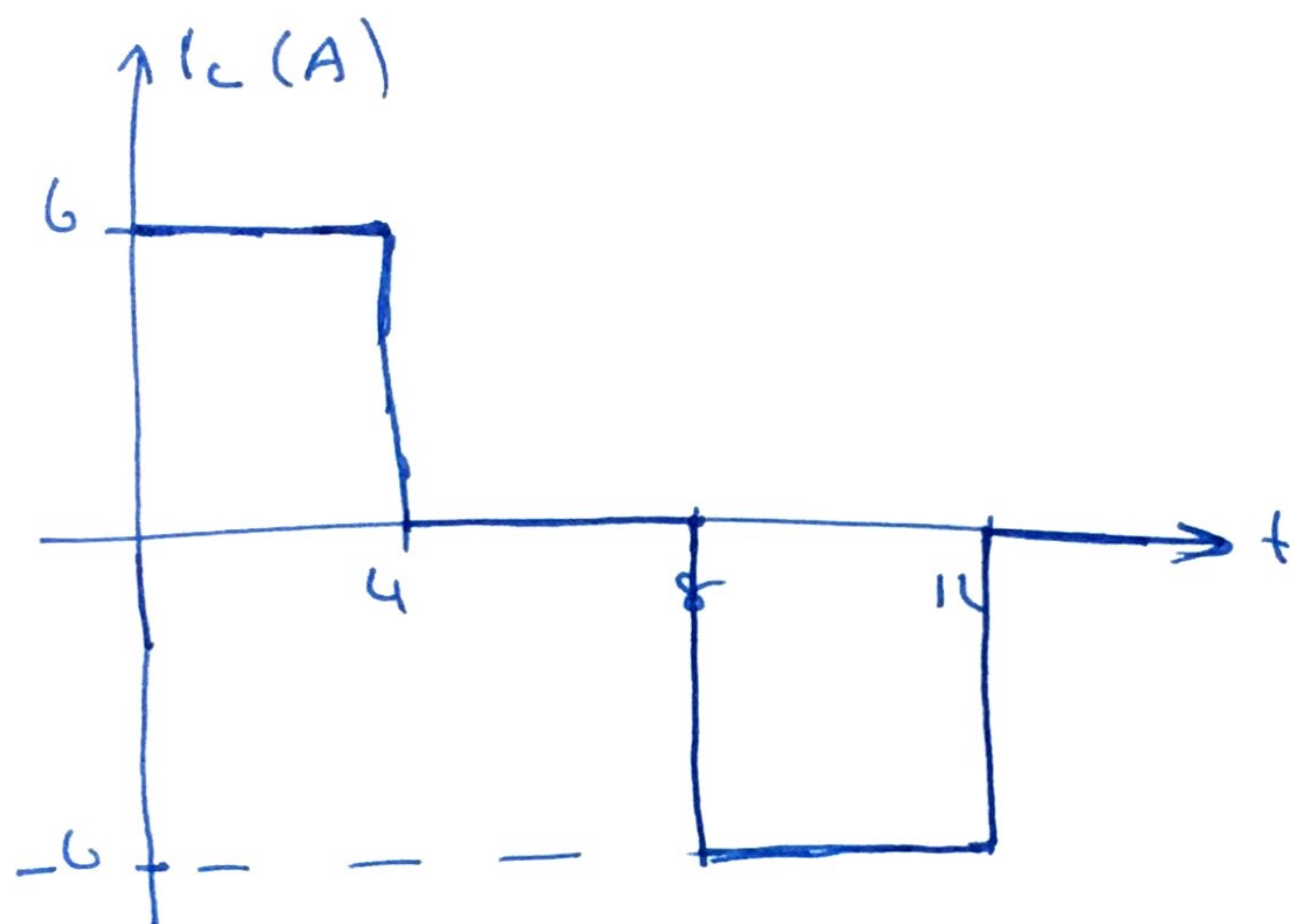

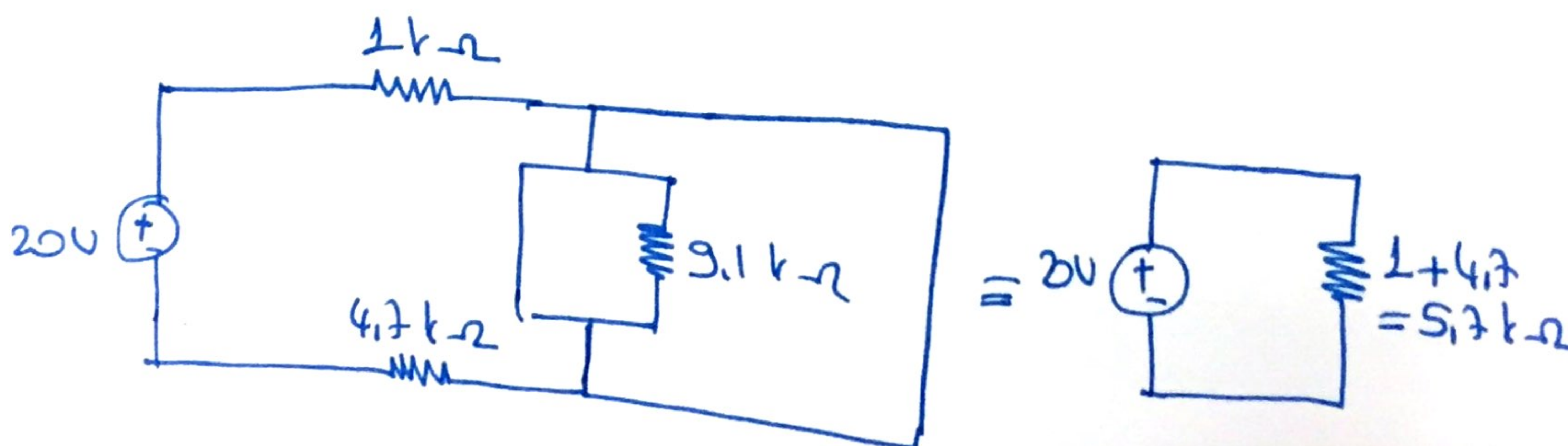- ④ Under DC condition inductance behaves as if short circuit then the circuit becomes.



⑤ $V_{out1} = \frac{-10}{j5} \times (-j5) = 10 \text{ V}$


$$V_{out2} = \frac{-10}{-j5} \times 10 = j2 \times 10 = -j20 = 20 \angle -90^\circ$$

$$\textcircled{6} \quad V_s(t) = 12 \sin(100t - 45^\circ) = 12 \cos(100t - 45 - 90^\circ) \\ = 12 \cos(100t - 135^\circ)$$

$$V_s = 12 \angle -135^\circ$$

$$X_L = j\omega L = j100 \times 5 \times 10^{-3} = j0.5 \, \Omega$$
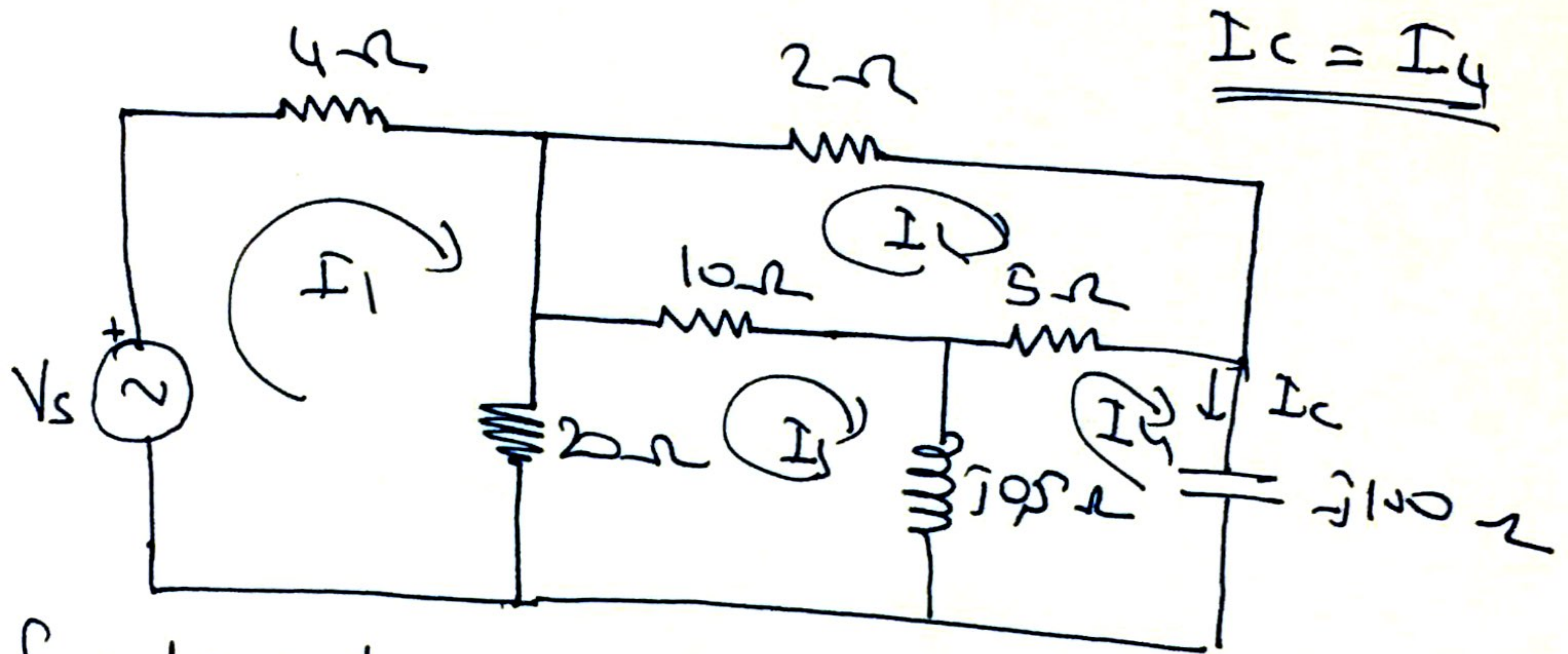
$$X_C = \frac{1}{j\omega C} = \frac{1}{j100 \times 100 \times 10^{-6}} = -j100 \, \Omega$$



for Loop 1

$$-V_s + 4 I_1 + 20(I_1 - I_3) = 0$$

$$* 24 I_1 - 20 I_3 = 12 \angle 435^\circ \quad \dots$$

for Loop 2

$$2 I_2 + 10(I_2 - I_3) + 5(I_2 - I_4) = 0$$

$$* 17 I_2 - 10 I_3 - 5 I_4 = 0$$

for Loop 3

$$20(I_3 - I_1) + 10(I_3 - I_2) + j0.5(I_3 - I_4) = 0$$

$$* (30 + j0.5) I_3 - 20 I_1 - 10 I_2 - j0.5 I_4 = 0 \quad *$$


for Loop 4.

$$j0,5(I_1 - I_3) + 5(I_1 - I_2) - j100I_4 = 0$$

$$*(5 - j99,5)I_1 - j0,5I_3 - 5I_2 = 0$$

$$\begin{bmatrix} 24 & 0 & -20 & 0 \\ 0 & 17 & -10 & -5 \\ -20 & -10 & 30 + j0,5 & -j0,5 \\ 0 & -5 & -j0,5 & 5 - j99,5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 12 \angle -135^\circ \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

(7)

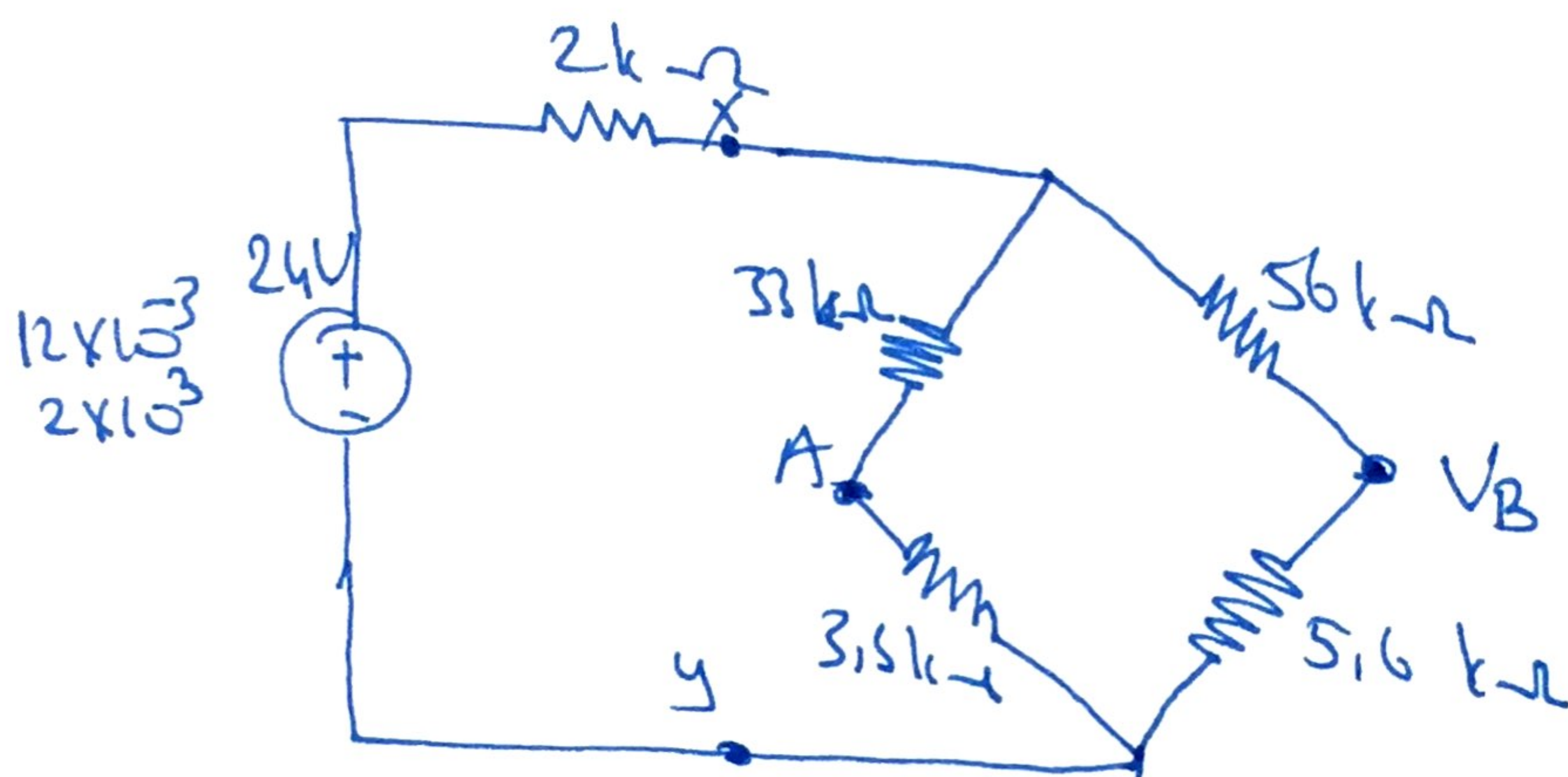

$$R_{eq} = \frac{36,3 \times 61,6}{36,3 + 61,6} = 22,84 \text{ k}\Omega$$


$$V_{xy} = \frac{22,84}{22,84 + 2} \times 24 = 20,42 \text{ V}$$

$$V_A = \frac{3,3}{36,3} \times 20,42 = 1,86 \text{ V}$$

$$V_B = \frac{5,6}{61,6} \times 20,42 = 1,86 \text{ V} \quad V_{TH} = 0 \text{ V}$$


then $P_{rs} = \underline{\underline{0 \text{ Watt}}}$

④ At $t = 0^-$ S1 is closed S2 is open

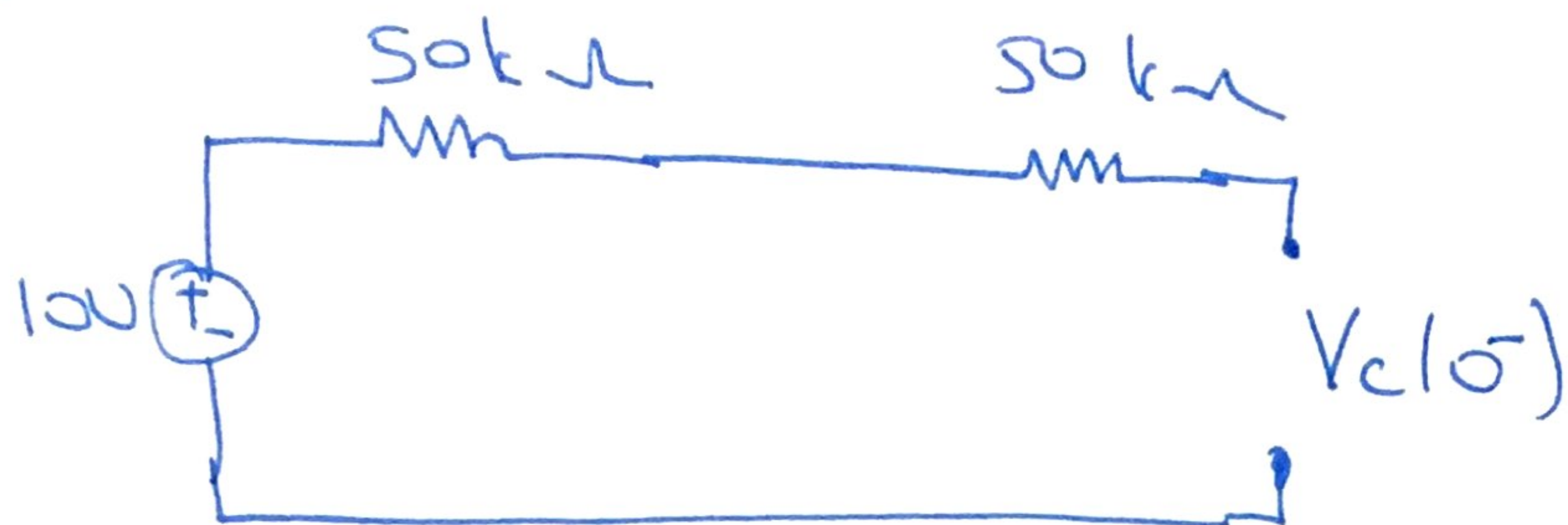

$$V_c(0^-) = 10 \text{ V.}$$

At $t = 0^+$

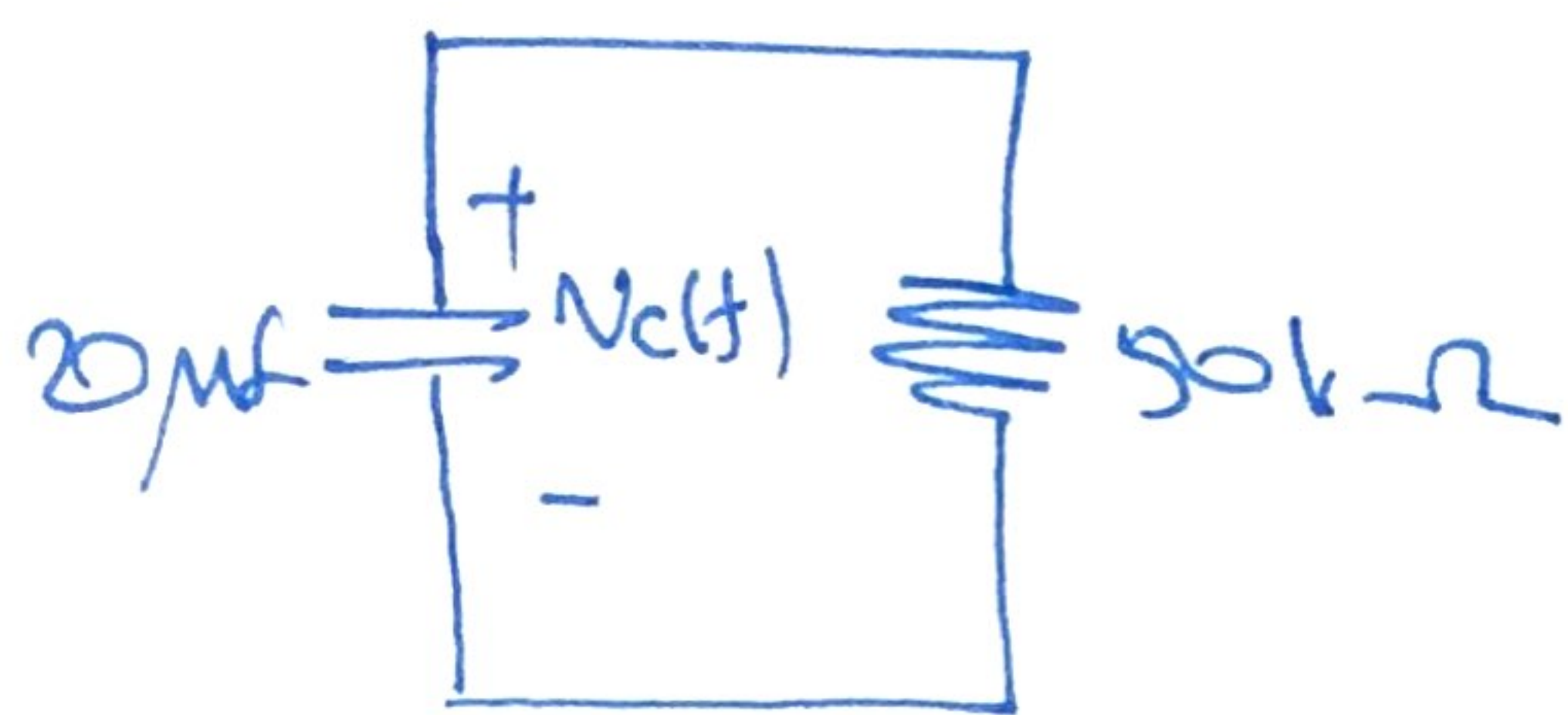

$$V_c(t) = V_0 e^{-t/RC}$$

$$\frac{1}{RC} = \frac{1}{50 \times 10^3 \times 20 \times 10^{-6}}$$

$$\frac{1}{RC} = \frac{1}{1000 \times 10^{-3} \times 10^{-6}} = 1$$

$$V_c(t) = 10 e^{-t}$$

a. $5 = 10 e^{-t} \Rightarrow \ln\left(\frac{5}{10}\right) = -t$

$$t = -\ln(0.5) = 0.693 \text{ s} = \underline{\underline{693 \text{ ms}}}$$

b. $W(0) = \frac{1}{2} \cdot 20 \times 10^{-6} \times 10^2 = 2 \text{ mJ}$

$$\frac{3}{4} W(0) = \frac{1}{2} C \cdot V_c(t)^2$$

$$\frac{3}{4} = e^{-2t} \Rightarrow t = -\ln\left(\frac{3}{4}\right) = 0.144 \text{ s}$$

$$= \underline{\underline{144 \text{ ms}}}$$