



Name, Surname :  
 Number :  
 Course Code : BLM1612  
 Course Name : CIRCUIT THEORY  
 Exam : ☐ Quiz ☐ Midterm ☒ Final  
 Date : 12.02.2017

**Please make sure to write your name and student number on each paper that you have used**

Question Number	1	2	3	4	5	6	7	Total
Mark								

**Note: Exam duration is 120 minutes only and max 2 papers can be used.**

### QUESTIONS

1. For the network of Fig. 1, find the total impedance  $Z_T$ .

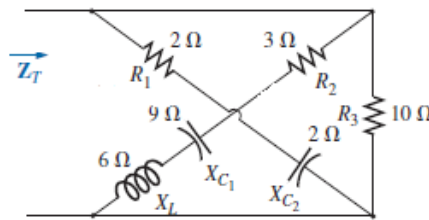


Fig. 1

2. Find the average power delivered to  $R_4$  in Fig. 2.

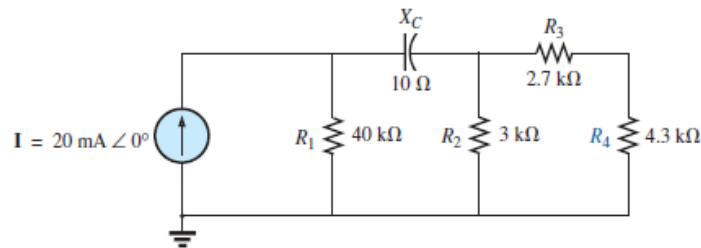


Fig. 2

3. For the network in Fig. 3, find the currents  $I_1$  and  $V_1$  in phasor form.

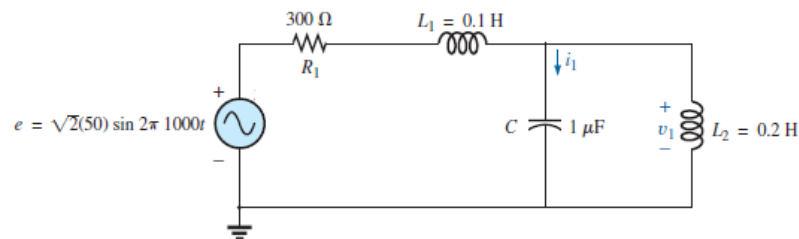


Fig. 3

4. Find the total inductance of the circuit of Fig. 4.

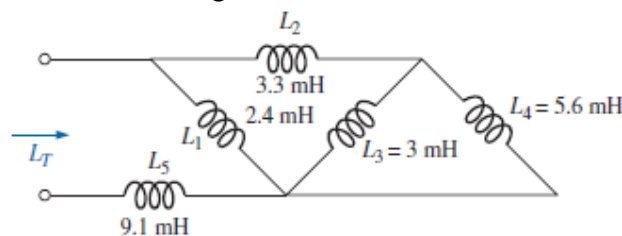


Fig. 4

5. For the circuit in Fig. 5; find the mathematical expression for the transient behavior of  $v_C$ ,  $i_C$ , and  $v_R$  if the switch is closed at  $t = 0$  s.

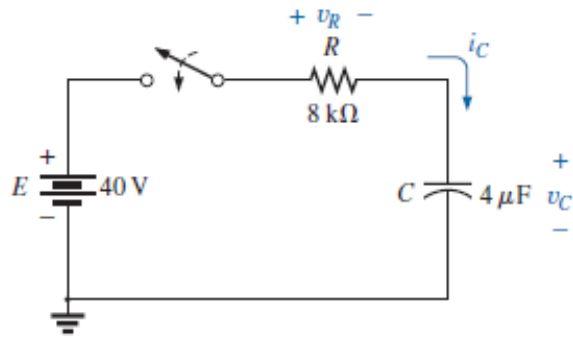


Fig. 5

6. Find the waveform for the average current if the voltage across the  $2 \mu\text{F}$  capacitor is as shown in Fig. 6.

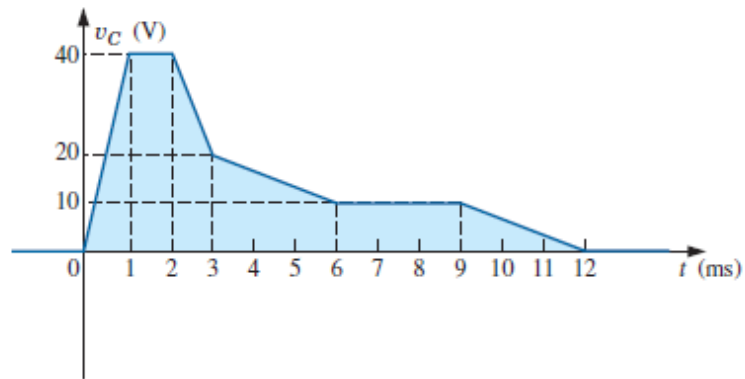


Fig. 6

7. For the multiple ladder configuration in Fig. 7, determine  $I$ .


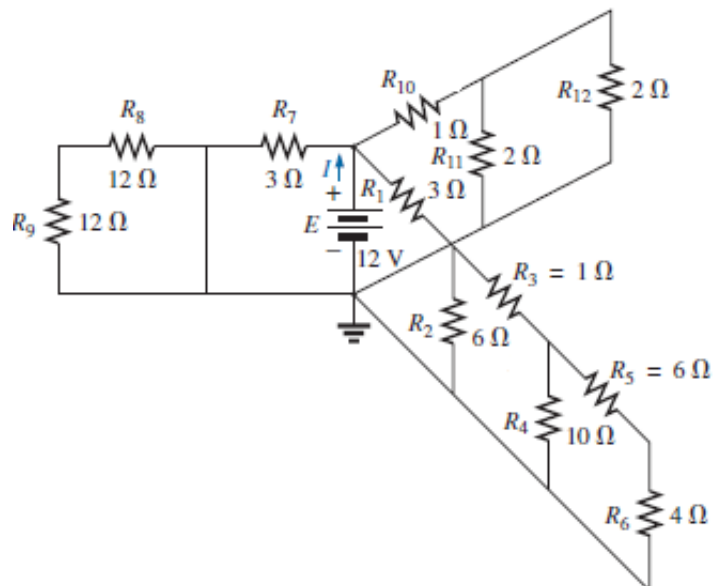


Fig. 7

①

ANSWER KEY

$$Z_T = \frac{V_s}{I}$$

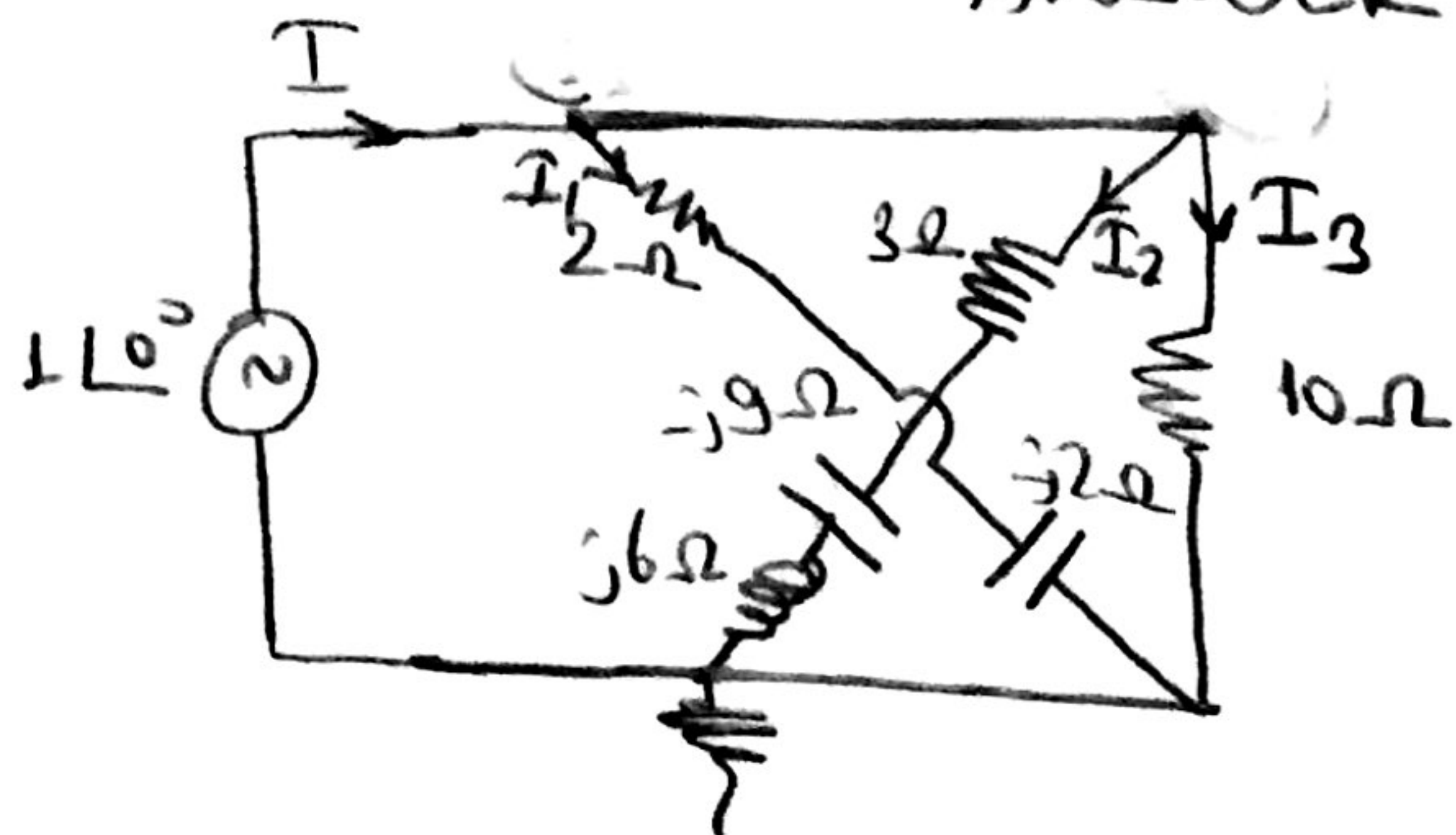

$$I = I_1 + I_2 + I_3$$

$$I_1 = \frac{1 \angle 0^\circ}{2 - j2} = \frac{1 \angle 0^\circ}{2\sqrt{2} \angle -45^\circ}$$

$$I_1 = 354 \angle 45^\circ \text{ mA}$$


$$I_2 = \frac{1 \angle 0^\circ}{3 + j(6-9)} = \frac{1 \angle 0^\circ}{3 - j3} = \frac{1 \angle 0^\circ}{3\sqrt{2} \angle -45^\circ} = 236 \angle 45^\circ \text{ mA}$$

$$I_3 = \frac{1 \angle 0^\circ}{10} = 100 \angle 0^\circ \text{ mA}$$

$$I = I_1 + I_2 + I_3 = (100 + 250 + 166) + j(250 + 166) = 516 + j416$$

$$Z_T = \frac{V_s}{I} = \frac{1 \angle 0^\circ}{(516 + j416) \times 10^{-3}} = 1.52 \angle -38.89^\circ \Omega$$

②

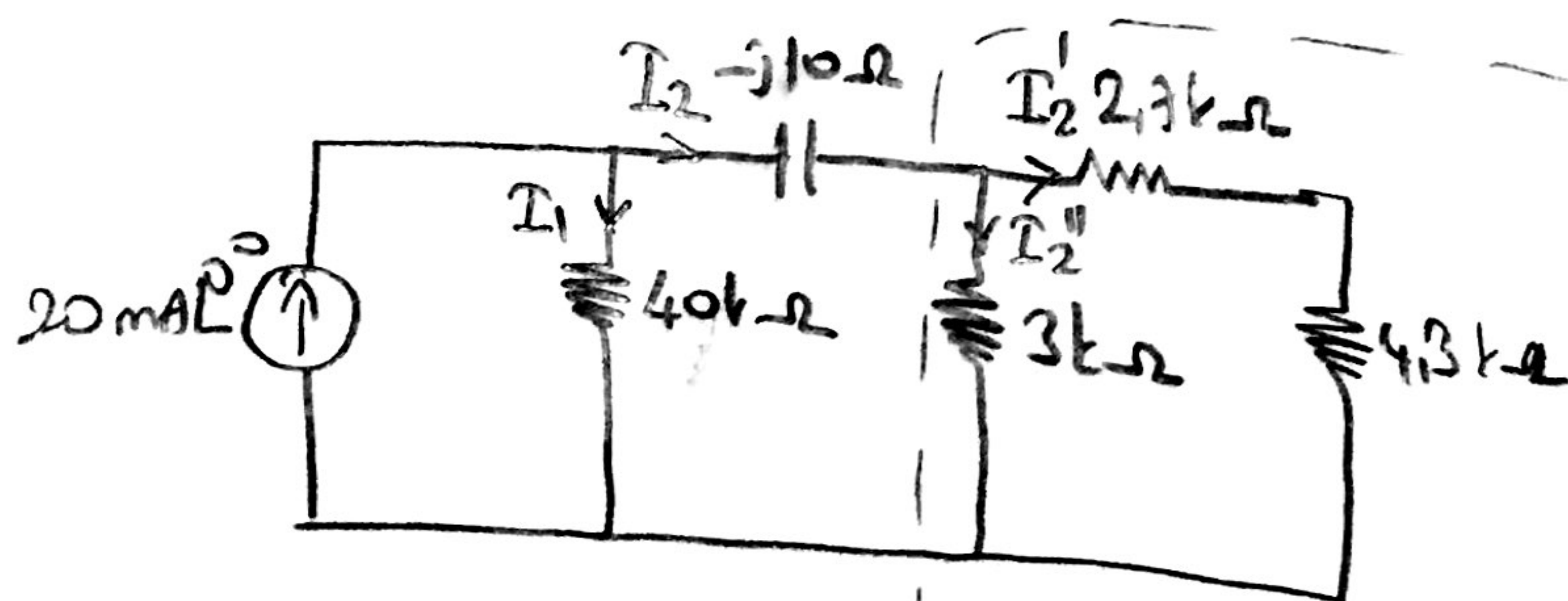

$$R_{eq} = 3k\Omega \parallel 7k\Omega = 2.1k\Omega$$

$$I_2 = \frac{40k\Omega}{40 + 2.1 - j10} \times 20 \angle 0^\circ \text{ mA}$$

$$= \frac{40,000}{40.002,1 - j10} \approx 19 \text{ mA}$$

$$I_2' = \frac{3}{10} \times 19 \text{ mA} \approx 5.7 \text{ mA}$$



$$P \simeq R(I_2')^2 = 4,3 \times 10^3 \cdot (5,7 \times 10^{-3})^2 = 139,7 \text{ mWatt}$$


$$(3) \quad e = \sqrt{2} \cdot 50 \cdot \sin 2\pi 1000t = \sqrt{2} \cdot 50 \cdot \cos(2\pi 1000t - 90^\circ)$$

$$\vec{E} = \sqrt{2} \cdot 50 \angle -90^\circ$$

$$jX_{L1} = 0,1 \times 2\pi \cdot 1000 = j200 \pi \Omega$$

$$-jX_C = \frac{-j}{2\pi \cdot 1000 \cdot 1 \times 10^{-6}} = -j159 \Omega$$
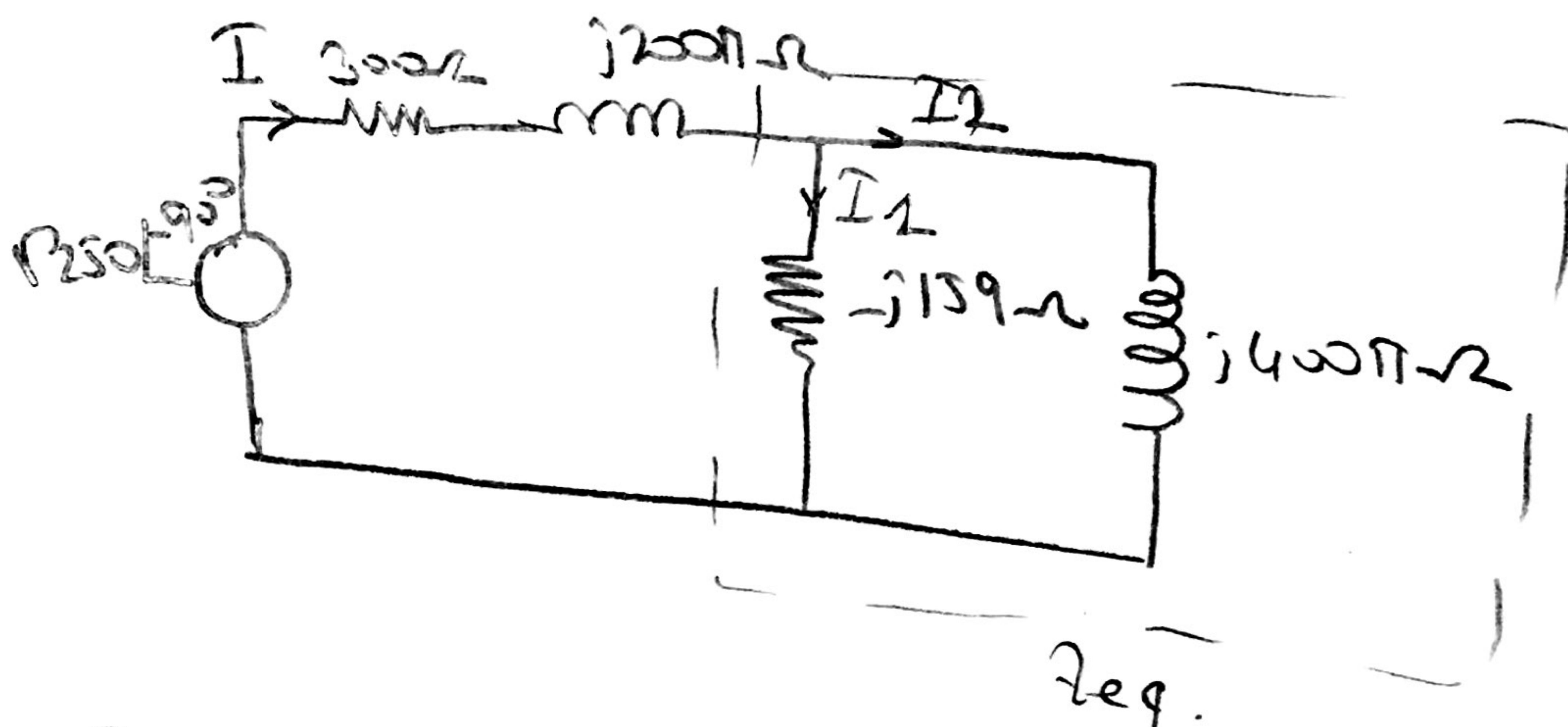
$$jX_{L2} = 0,2 \times 2\pi \cdot 1000 = j400 \pi \Omega$$



$$Z_{eq} = \frac{-j159 \times j400\pi}{j400\pi - j159} = \frac{199,704}{-j1097}$$

$$Z_{eq} = j \cdot 182,04 \Omega$$

$$I = \frac{\sqrt{2} \cdot 50 \angle -90^\circ}{300 + j(200\pi + 182,04)} = \frac{\sqrt{2} \cdot 50 \angle -90^\circ}{300 + j(810,04)}$$

$$I = \frac{\sqrt{2} \cdot 50 \angle -90^\circ}{863,81 \angle 69,67^\circ} \simeq 82 \angle -159,67^\circ \text{ mA}$$



$$I_1 = \frac{j400\pi}{j400\pi - j159} \times I$$

$$= \frac{j400\pi}{j1097} \cdot 82 \angle -159,67^\circ \approx 102,86 \angle -159,67^\circ \text{ mA}$$

$$V_1 = j400\pi \times (I - I_1)$$

$$= j400\pi \times (-20,85 \angle -159,67^\circ) \times 10^{-3}$$

$$= 400\pi \angle 90^\circ \cdot 20,85 \angle -159,67^\circ - 90^\circ \times$$

$$= 26,19 \angle -159,67^\circ \text{ V}$$

$$\textcircled{4} \quad L_T = L_1 \parallel (L_2 + (L_3 \parallel L_4)) + L_5$$

$$= 2,4 \parallel \left( 3,3 + \frac{3 \times 5,6}{8,6} \right) + 9,1$$

$$= \frac{2,4 \times 5,25}{7,65} + 9,1 = \underline{\underline{10,75 \text{ mH}}}$$

$$\textcircled{5} \quad V_c(t) = V_{cn}(t) + V_{cf}(t)$$

$V_{cf}(t) = V_c(t \rightarrow \infty) = E$  since  $C$  behaves as if open circuit.

$$V_{cn}(t) = A \cdot e^{-t/\tau}$$

$$\tau = R \cdot C = 8 \times 10^3 \times 4 \times 10^{-6}$$

$$\tau = \frac{32 \times 10^{-3}}{31,25} \text{ s}$$

$$V_{cn}(t) = A \cdot e^{-t/(32 \times 10^{-3})} = A \cdot e^{-31,25 t}$$

$$V_{C(t)} = E + A e^{-31.25t}$$

At  $t=0$   $V_C(0)=0$  then

$$0 = E + A \Rightarrow A = -E$$

$$V_{C(t)} = E \cdot (1 - e^{-31.25t}) \text{ V} = 40(1 - e^{-31.25t})$$

$$i_C = \frac{40 e^{-31.25t}}{8 \times 10^3} \quad A = 5 e^{-31.25t} \text{ mA}$$

$$V_R = 40 e^{-31.25t} \text{ V}$$

(b)  $i_C = C \cdot \frac{dV_C}{dt} = C \cdot \text{slope} = C \cdot m$

$0 < t < 1 \text{ ms}$

$$m = \frac{40 - 0}{(1 - 0) \times 10^{-3}} = 40 \times 10^3$$

$$i_C = 2 \times 10^{-6} \times 40 \times 10^3 = 80 \text{ mA}$$

$1 < t < 2 \text{ ms}$

$$m = 0 \Rightarrow i_C = 0$$

$2 < t < 3 \text{ ms}$

$$m = \frac{20 - 40}{(3 - 2) \times 10^{-3}} = -20 \times 10^3$$

$$i_C = 2 \times 10^{-6} \times (-20 \times 10^3) = -40 \text{ mA}$$

$3 < t < 6 \text{ ms}$

$$m = \frac{10 - 20}{(6 - 3) \times 10^{-3}} = -\frac{10}{3} \times 10^3$$

$$i_C = 2 \times 10^{-6} \times \left(-\frac{10}{3} \times 10^3\right) = -6.67 \text{ mA}$$




$$6 \mu s < t < 9 \text{ ms}$$

$$m = 0 \Rightarrow i_c = 0$$


$$9 \mu s < t < 12 \text{ ms}$$

$$m = \frac{0 - 10}{(12 - 9) \times 10^3} = -\frac{10 \times 10^3}{3}$$
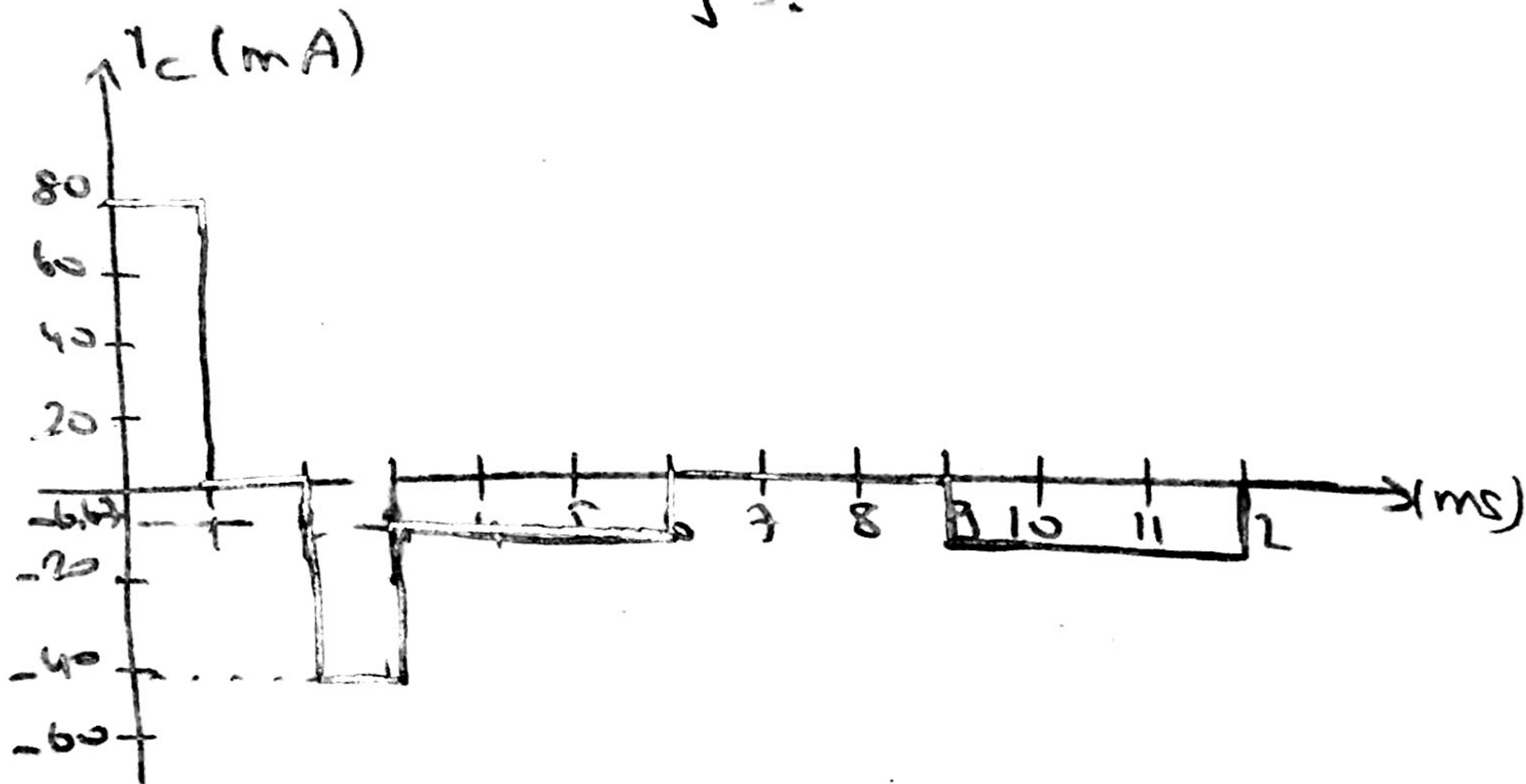
$$i_c = 2 \times 10^{-6} \times \left(-\frac{10}{3} \times 10^3\right) = -6.67 \text{ mA}$$



⑦

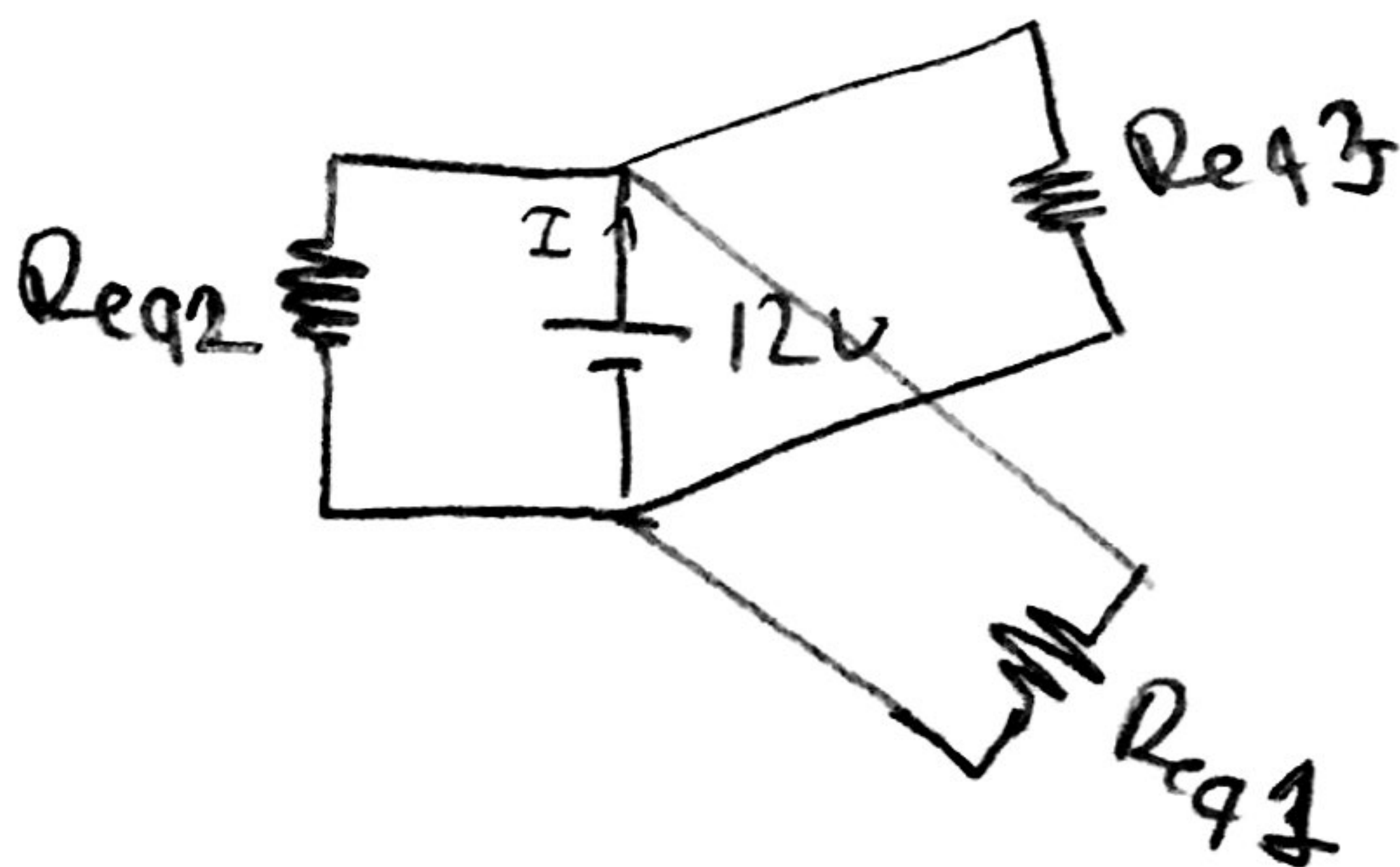

$$\begin{aligned} R_{eq1} &= R_1 + R_2 \parallel (R_3 + R_4 \parallel (R_5 + R_6)) \\ &= 3 + 6 \parallel (1 + 10 \parallel (6 + 4)) \\ &= 6 \Omega \end{aligned}$$

$$R_{eq2} = R_7 = 3 \Omega$$

$$R_{eq3} = R_{10} + R_{11} \parallel R_{12} = 1 + 2 \parallel 2 = 2 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_{eq1}} + \frac{1}{R_{eq2}} + \frac{1}{R_{eq3}} = \frac{1}{6} + \frac{1}{3} + \frac{1}{2}$$

$$R_{eq} = 1 \Omega$$

$$I = \frac{E}{R_{eq}} = \frac{12}{1} = 12 \text{ A.}$$